

Milestone 4 - Mechaminds

Here is a summary of our PIC24F16KA301 pinout:

Component	Pic Pin #	Pic pin #	Ccomponent
MCLR	1	20	3.3 V
A/I (QRD for ball color sensing)	2	19	GND
A/I (QRD (reading bar codes))	3	18	A/I (ultrasonic sensor(right))
PWM (left stepper motor driver)	4	17	A/I (QRD (line detection 1))
PWM (large servo)	5	16	A/I (QRD (line detection 2))
D/O (left stepper motor driver)	6	15	A/I (photodiode (line detection 3))
D/O (mosfet for laser)	7	14	PWM (right stepper motor driver)
A/I (QRD for T junction recognition)	8	13	D/O (right stepper motor driver)
A/I (IR photodiode laser detection)	9	12	D/I (IR proximity sensor front)
D/O (mosfet to trigger nerf solenoid)	10	11	D/I (IR photodiode service station)

List of Components Used

- 1x US -016 Ultrasonic Distance Sensor (Analog)
- 6x QRD Sensor (QRD1114)
- 2x NEMA 17 Stepper Motor (SY42STH38) and Pololu MP6500 Motor Driver and Carrier Board
- 1x Longrunner MG996R Servo
- 2x MOSFET Transistor (IRLB8748PBF)
- 1x 650nm Laser Diode
- 1x IR Proximity Sensor
- 2x IR Photodiode
- 1x LiFePO4 Battery Pack
- 1x 12V Actuated Solenoid
- 1x 5V Buck Converter

Please see pages below for detailed schematic of circuit design:

US - 016 Ultrasonic Distance Sensor (Analog)




VCC 3.3V - 5.0V
- Max Current 3.8mA

1 A/I P:n [RB15 (#18)]

→ Buck converter
12V - 5V

QRD Sensor (QRD1114)

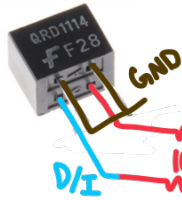


VCC 3.3V
- Max Current 20mA

6 A/I P:ns

RB 14 (#17)
RB 13 (#16)
RB 12 (#15)
RA1 (#3)
RA0 (#2)
RA3 (#8)

NEMA 17 Stepper Motor (SY42STH38) and Pololu MP6500 Motor Driver and Carrier Board

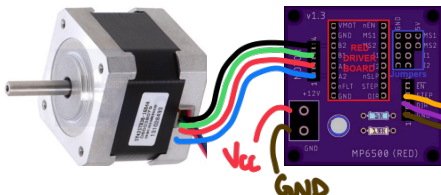

VCC 12.0V
- Max Current 1680mA
(Carrier board limits this)

2 PWM P:ns [RB0 (#4)
RA6 (#14)]

2 D/O P:ns [RB2 (#6)
RA9 (#13)]

Longrunner MG996R Servo




VCC 4.8V - 7.2V
- Operating current 700mA

→ Buck converter
12V - 5V

1 PWM P:n [RB1 (#5)]

MOSFET Transistor (IRLB8748PBF) and 650nm Laser Diode

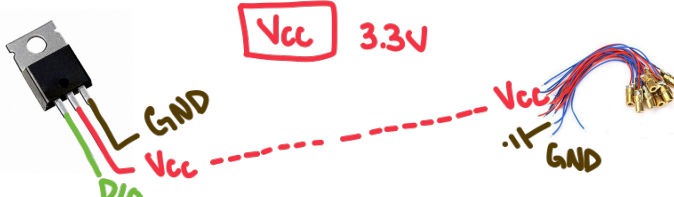


VCC 3.3V

1 D/O P:n [RA2 (#7)]

1 D/O P:n [RA4 (#10)]

IR Proximity Sensor

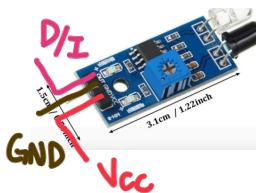


VCC 3.3V - 5.0V

→ Buck converter
12V - 5V

1 D/I P:n [RB8 (#12)]

IR Photodiode

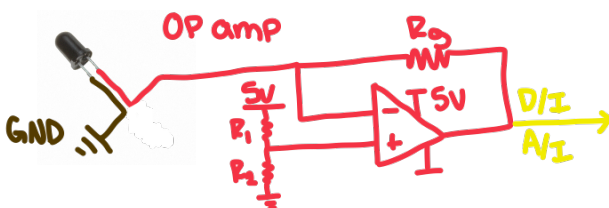

1 A/I P:n [RB4 (#9)]


1 D/I P:n [RB7 (#11)]

LiFePO4 Battery Pack




12V Directly supply motors } PCB to microcontroller

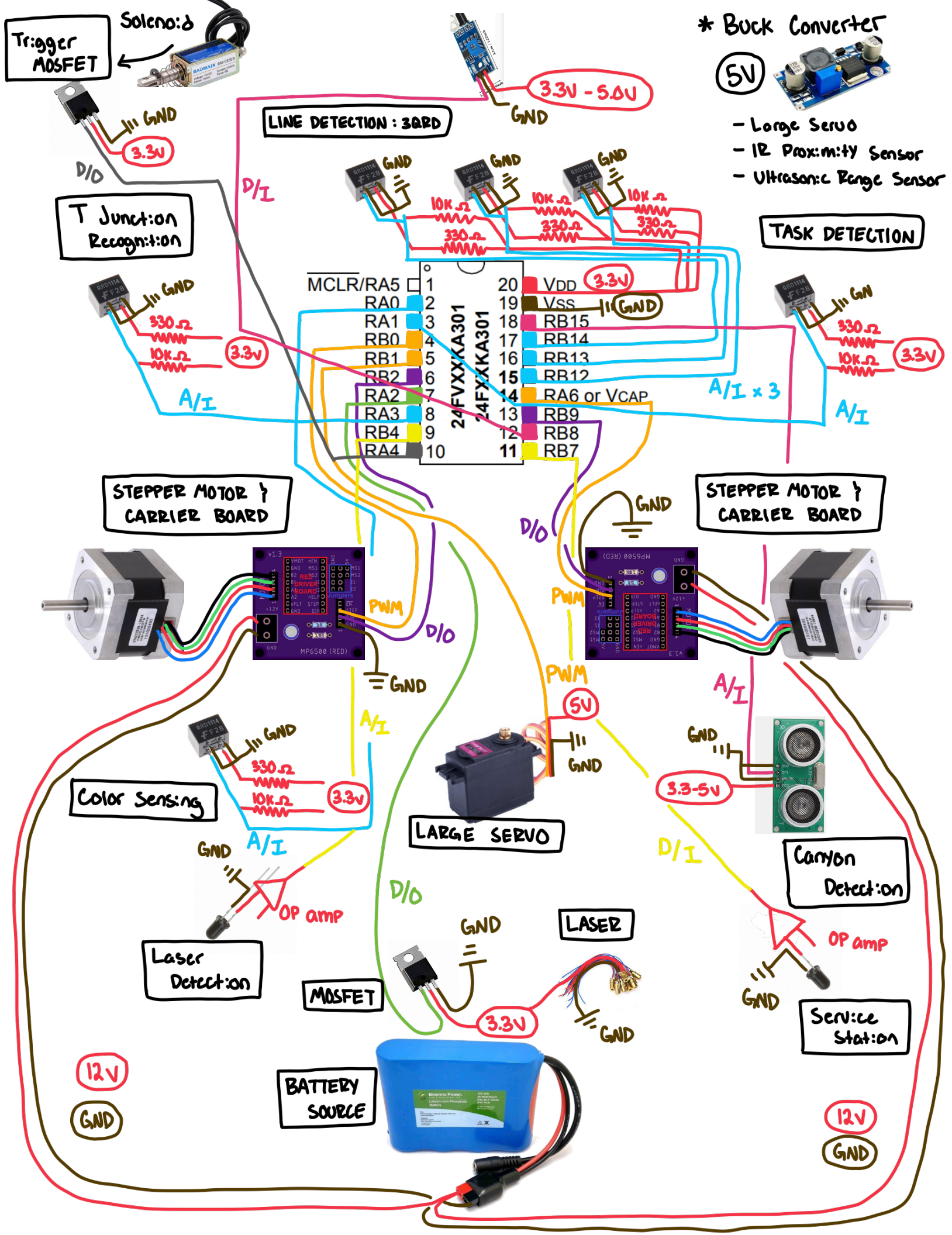5V Voltage regulator (Buck converter) for { Large Servo
IR Proximity
Ultrasonic Range




Milestone 4 Schematics

Solenoid Trigger Mosfet

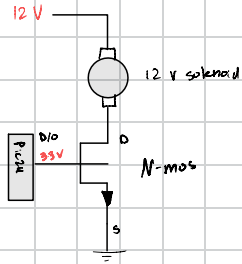


QRD Circuit

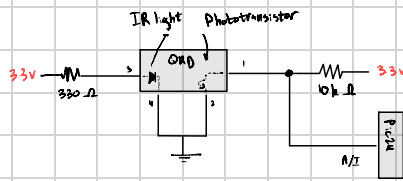

Note: - Pins 1-4 are labeled on datasheet.


- The dotted lines within the QRD box represents built-in circuitry provided

IR Proximity Sensor

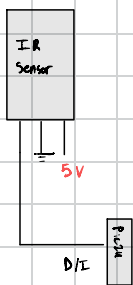


Note: 5v comes from buck converter

Large Servo

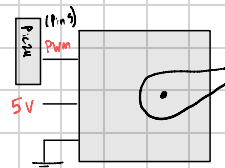

Note: 5v comes from buck converter

Photodiode

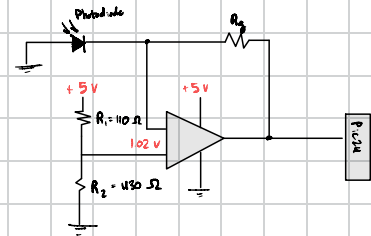


Note: - 5v comes from buck converter


- R_3 will be experimentally picked

- For laser detection, use on A/I pin
- For service station detection, use INTO

Analog Ultrasonic

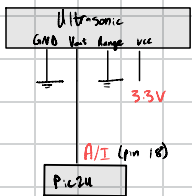

Laser

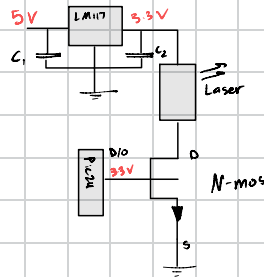

Note:

- $C_1 = 10\mu F$
- $C_2 = 100\mu F$
- Using 3.3V regulator

Stepper Motors

- As drawn in previous pages

General Notes:

- All 12v applications come from battery pack
- All 5v applications come from buck converter
- All 3.3v applications come from an output pin on PIC24, unless noted otherwise